

# System Synthesis and Modeling

CSCE 3953

Fall 2018

Mon, Wed, Fri (9:40 AM – 10:30 AM)

## Final Project

## Simple Microcontroller Design

10-06-2018

Suhail Basalama

010786839

[sebasala@email.uark.edu](mailto:sebasala@email.uark.edu)

## Project Objective

The goal of this project is to integrate all the skills learned in this class to build a whole system in Verilog. A microcontroller is a perfect system that involve both sequential and combinational logic like registers, decoders, ALU. This project aims at giving us experience with Finite State Machines to control all the internal signals of the microcontroller. Merging all these parts together create a complex structure that needs careful observation and debugging skills. Finally, another objective is to simulate and synthesize our circuits using CAD tools like ModelSim and Synopsys to produce a performing microcontroller.

## Design Methodology

### Nomenclature and Standards

Predicting the complexity of this project, I decided to set a constant nomenclature standard. I considered the Memory Module and the Bus to be masters, and I set all other components as slaves. The word “read” means that the bus or the memory is reading from a slave module; similarly, the word “write” means that the bus is writing into that slave module. If the memory module is the master, I added “mem” as a prefix to the word “read” or “write” like “mem\_read” meaning that the memory is reading one of the slave modules. I also set the ports in a constant order for all my modules, where I start with “clk”, “reset” and then all other ports.

### Ports

I made my microcontroller synchronous with rising edge for all my modules except the decoder which does not have a clk. For all my modules I added an active high asynchronous reset to reset all the registers to 0. Top module has five ports as follow: clk, reset, input\_pin, output\_pin, input\_enable. Other modules have different ports based on their functionality.

### Top

My top module starts with including all the modules from the whole hierarchy using the command (``include`). Next is declaring my ports. After that, I added my bus as a 16-bit wires and all other wires to connect the different modules. Then, I added all the seven FSMs to produce the control signals. Next, I ORed all my control signals to put them into the microcontroller

components like registers. After that I added other components with the proper signals assigned to them.

## Finite State Machines

I decided to create seven different Moore FSMs to produce all the control signals which are:

### 1. Fetch:

State1: PC(read) and MAR(write)  
State2: MAR(mem\_read) and MEM(RW,EN)  
State3: wait for memory MEM(MFC)  
State4: MDR(mem\_write)  
State5: MDR(read) and IR(write)  
Done: PC(increment) and done = 1

### 2. Move

State1: Ri(write) and Rj(read)  
Done: done = 1

### 3. Movi

State1: FSM(read) and Ri(write)  
Done: done = 1

### 4. ALU

State1: Ri(read) and ALU(writeIN1)  
State2: Rj(read) and ALU(writeIN2)  
State3: ALU(alu\_out\_en) and ALU(opControl)  
State4: ALU(read) and Ri(write)  
Done: done = 1

### 5. ALUI

State1: Ri(read) and ALU(writeIN1)  
State2: FSM(read) and ALU(writeIN2)  
State3: ALU(alu\_out\_en) and ALU(opControl)  
State4: ALU(read) and Ri(write)  
Done: done = 1

### 6. Store


State1: Ri(read) and MDR(write)  
State2: Rj(read) and MAR(write)  
State3: MDR(mem\_read) and MEM(!RW) and MEM(EN)  
Done: done = 1

### 7. Load

State1: Ri(read) and MAR(write)  
State2: MAR(mem\_read) and MEM(RW) and MEM(EN)  
State3: wait for MFC  
State4: MDR(mem\_write)  
State5: MDR(read) and Rj(write)  
Done: done = 1
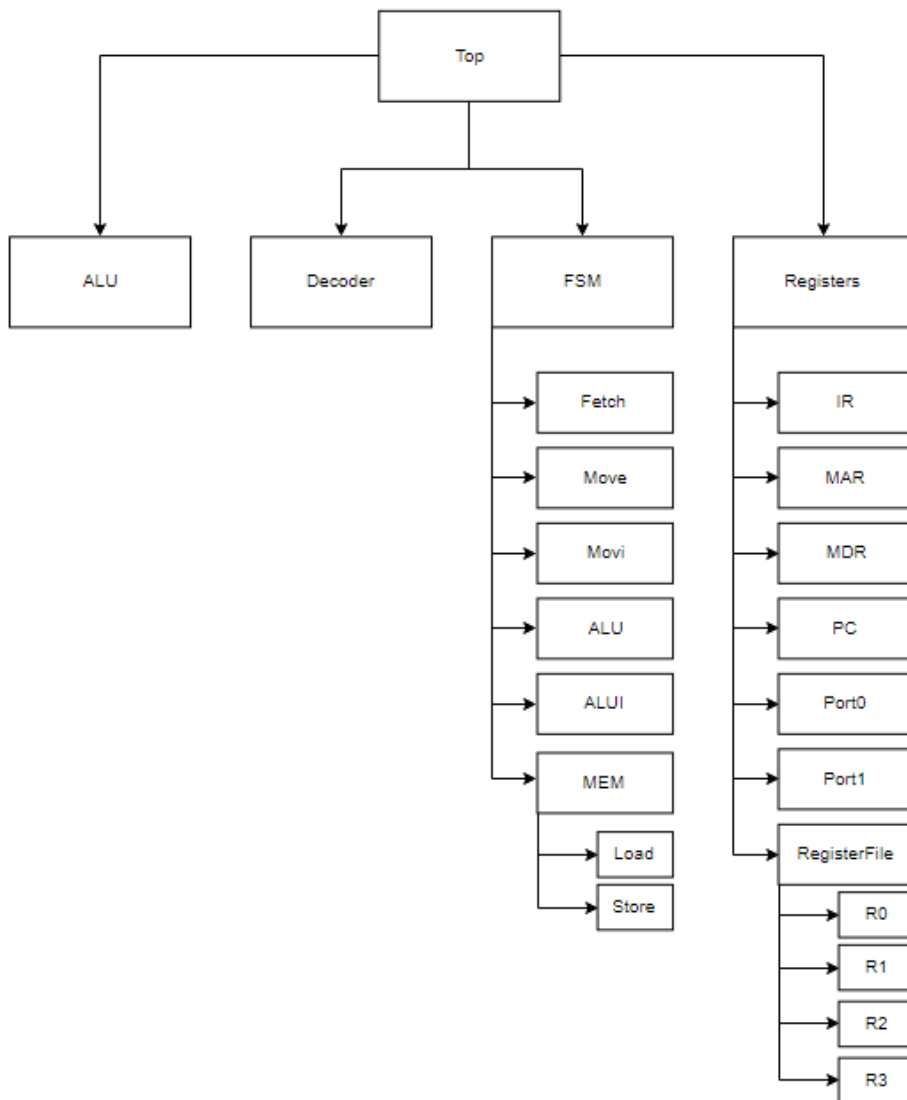
## Project File Structure

I created my modules in a hierarchical structure as shown in the diagram below:



## Instruction Set with Machine Code

Add	Ri, Rj	0000	Addi Ri, #	1000	Load (Ri), Rj	1010
Sub	Ri, Rj	0001	Subi Ri, #	1001	Store Ri, (Rj)	1011
Not	Ri	0010	Movi Ri, #	1111		
And	Ri, Rj	0011				
Or	Ri, Rj	0100				
Xor	Ri, Rj	0101				
Xnor	Ri, Rj	0110				
Mov	Ri, Rj	0111				

Ri = i in 6-bit binary  
Rj = j in 6-bit binary  
P0 = 000100  
P1 = 000101

## Assumptions

1. Instructions can take as many Clock cycles as necessary.
2. Asynchronous active high reset.
3. All modules are positive edge clock triggered.
4. One memory cell only, so a max of one store can be used.
5. P1 is already integrated in the FSMs, but it can be enabled from the top level as well using the input\_enable signal.
6. ALU opControl signals are:  
parameter ADD = 0;  
parameter SUB = 1;  
parameter NOT = 2;  
parameter AND = 3;  
parameter OR = 4;  
parameter XOR = 5;  
parameter XNOR = 6;

## Simulation Method

I used the instructions provided in the document which translate to machine code as follows:


```
010786839
MOVI  R1, #15      1111 000001 010101
MOVI  R2, #2F      1111 000010 101111
ADD   R1, R2       0000 000001 000010
MOV   P0, R1       0111 000100 000001
XOR   R2, R1       0101 000010 000001
INV   R2           0010 000010 000000
STORE P0, (R2)     1011 000100 000010
LOAD  (R2), R0     1010 000010 000000
```

The microcontroller can perform all the instructions, and Port 1 is integrated as well.
 
## Results


Fetch instruction starts by moving the data from the Program Counter (PC) register to the Memory Address (MAR) register, and the bus will contain the PC value at this stage; second, it moves the data from MAR to the memory and wait for MFC to drop so the bus will be in high impedance in this stage; third, the memory writes the data into the Memory Data Register (MDR) register, and the bus is still in high impedance because this transition is between MDR and MEM; fourth, the data (instruction in this case) is released from the MDR to the IR through the bus, so the bus will have the Instruction at this stage. That was the fetch cycle and it applies for all the instructions.

Here is a general overview of the all the instructions:



Instruction 1 (MOVI R1, #15      1111 000001 010101)

 
Fetching the instruction is the same as explained above. When fetch done, MOVI FSM is started. Next the signal R1\_write is high and the FSM internal tri-state buffer lets the immediate value to be outputted to the bus through which then goes through the bus to R1.






Instruction 2 (MOVI R2, #2F 1111 000010 101111)

 Fetching the instruction is the same as explained above. When fetch done, MOVI FSM is started. Next the signal R2\_write is high and the FSM internal tri-state buffer lets the immediate value to be outputted to the bus through which then goes through the bus to R2.




Instruction 3 (ADD R1, R2 0000 000001 000010)

Fetch is the same as explained before. Then the ALU FSM starts and it asserts Ri (R1) and ALU\_in1 at the same time allowing the data to go through the bus from R1 to ALUreg1. Next, the same happens with Rj (R2) and the data moves to ALU\_in2. After that the ALU\_opControl is generated by the FSM (000) and sent to the ALU which evaluates the result and the ALU\_out reg is enabled to store the result. Next, the result is allowed to go to the bus by asserting ALU\_read (meaning the bus will read the ALU) and asserting the destination Register (R1\_write) at the same time.

 


Instruction 4 (MOV P0, R1 0111 000100 000001)

 The fetch is the same here as well. When Move FSM starts both signals P0\_write and R1\_read are asserted at the same time, which means that the bus will read from R1 and write to P0.




Instruction 5 (XOR R2, R1 0101 000010 000001)

Fetch is the same as explained before. Then the ALU FSM starts and it asserts Ri (R2) and ALU\_in1 at the same time allowing the data to go through the bus from R2 to ALUreg1. Next, the same happens with Rj (R1) and the data moves to ALU\_in2. After that the ALU\_opControl is generated by the FSM (101) and sent to the ALU which evaluates the result and the ALU\_out reg is enabled to store the result. Next, the result is allowed to go to the bus by asserting ALU\_read (meaning the bus will read the ALU) and asserting the destination Register (R2\_write) at the same time.

 


Instruction 6 (INV R2 0010 000010 000000)

Fetch is the same as explained before. Then the ALU FSM starts and it asserts Ri (R2) and ALU\_in1 at the same time allowing the data to go through the bus from R2 to ALUreg1. Next, the same happens with Rj (R0 or any other register will not affect the result) and the data moves to ALU\_in2. After that the ALU\_opControl is generated by the FSM (010) and sent to the ALU which evaluates the result and the ALU\_out reg is enabled to store the result. Next, the result is allowed to go to the bus by asserting ALU\_read (meaning the bus will read the ALU) and asserting the destination Register (R2\_write) at the same time.

 


Instruction 7 (STORE P0, (R2))      1011 000100 000010)

Fetch is the same. After that, the data moves from the Ri (P0) to the memory data register MDR by asserting P0\_read and MDR\_write at the same time. Next step is to copy the address from R2 to memory address register MAR by asserting R2\_read and MAR\_write simultaneously. Finally, the FSM enables the memory by setting EN high, and set RW to 0 to write to memory, and then wait for the data to be written into the memory which is indicated by MFC signal going to zero.

 

Instruction 8 (LOAD (R2), R0      1010 000010 000000)

For fetch, it is the same. And the load is almost the same with fetch except that load takes data from memory to another register other than IR. So, load FSM starts by sending the address from Ri (R0) to the memory address register MAR by asserting R2\_read and MAR\_write simultaneously. Then we send the data to memory by asserting EN and RW to read from memory and we wait for MFC to drop. The FSM then allow the data to be written to the MDR register by enabling MDR\_mem\_write. Finally, the FSM sends the data from MDR to Rj (R0) by asserting MDR\_read and R0\_write simultaneously.

 

## Analysis and Conclusion

This was an excellent project that combined all what we have learned in this class starting from implementing simple logic devices like registers and decoder, to more complex ones like ALU. It also had excellent examples to practice what we learned about Finite State Machines and how to use them in our designs in a practical way. In addition, one of the main aspects of this project is the complexity and how hardware systems can be very complicated even if it seems easy from the outside. Therefore, I learned a very important skill which is standardizing my naming and methodology so that I can handle large systems like this one. If I did not spend some time organizing the structure and design of my microcontroller, I would not be able to finish it in about four days. Finally, I did synthesize my registers and they work properly, but my FSMs have some issues after synthesis since I am raising my control signals for one clock cycle only, but I am planning to complete the synthesis process in the break and deploy my project to an FPGA to test it in reality.



## Source Code

### Top.v

```
`include "/FSM/Fetch/Fetch.v"
`include "/FSM/Move/Move.v"
`include "/FSM/Movi/Movi.v"
`include "/FSM/ALU_FSM/ALU_FSM.v"
`include "/FSM/ALUI_FSM/ALUI_FSM.v"
`include "/FSM/Mem_FSM/Store.v"
`include "/FSM/Mem_FSM/Load.v"
`include "/Registers/PC/PC.v"
`include "/Registers/MAR/MAR.v"
`include "/Registers/MDR/MDR.v"
`include "MEM.v"
`include "/Registers/IR/IR.v"
`include "/Registers/RegisterFile/R0.v"
`include "/Registers/RegisterFile/R1.v"
`include "/Registers/RegisterFile/R2.v"
`include "/Registers/RegisterFile/R3.v"
`include "/Decoder/Decoder.v"
`include "/ALU/ALU_pre.v"
`include "/Registers/Port0/Port0.v"
`include "/Registers/Port1/Port1.v"

module top(clk, reset, input_pin, output_pin, input_enable);

input clk, reset, input_enable;
input[15:0] input_pin;
output[15:0] output_pin;

wire[15:0] bus;

wire[15:0] MAR_to_MEM;
wire[15:0] MDR_to_MEM;
wire[15:0] MEM_to_MDR;

wire MFC;
wire PC_read, PC_increment;
wire MAR_write, MAR_mem_read;
wire MEM_RW, MEM_EN;
wire MDR_mem_write, MDR_read;
wire IR_write;
wire[15:0] out_to_decoder;
wire move_done, movi_done, ALU_done, ALUI_done, load_done, store_done;
```

```

wire start_fetch, start_move, start_movi, start_ALU, start_ALUI, start_load,
start_store;

wire R0_write, R0_read;
wire R1_write, R1_read;
wire R2_write, R2_read;
wire R3_write, R3_read;
wire P0_write, P0_read;
wire decode_done, fetch_done;

wire ALU_read;
wire[2:0] opControl;

wire[5:0] Ri, Rj;
wire[3:0] opCode;

wire[2:0] ALU_opControl, ALUI_opControl;

assign Rj = out_to_decoder[5:0];
assign Ri = out_to_decoder[11:6];
assign opCode = out_to_decoder[15:12];

assign start_fetch = reset || move_done || movi_done || ALU_done || ALUI_done ||
load_done || store_done;

Decoder Decoder_comp(fetch_done, opCode, start_move, start_movi, start_ALU,
start_ALUI, start_load, start_store);

reg flag = 1;
always@(PC_read)
if(bus==7) flag = 0;

Fetch Fetch_comp
(
    clk, reset, start_fetch && flag, MFC,
    PC_read, PC_increment,
    MAR_write_fetch, MAR_mem_read_fetch,
    MEM_RW_fetch, MEM_EN_fetch,
    MDR_mem_write_fetch, MDR_read_fetch,
    IR_write, fetch_done
);

Move Move_comp
(

```

```

    clk, reset, start_move, Ri, Rj,
    move_done,
    R0_write_move, R0_read_move,
    R1_write_move, R1_read_move,
    R2_write_move, R2_read_move,
    R3_write_move, R3_read_move,
    P0_write_move, P0_read_move,
                    P1_read_move
);

Movi Movi_comp
(
    clk, reset, start_movi, Ri, Rj,
    bus,
    movi_done,
    R0_write_movi,
    R1_write_movi,
    R2_write_movi,
    R3_write_movi,
    P0_write_movi
);

ALU_FSM ALU_FSM_comp
(
    clk, reset, start_ALU, opCode, Ri, Rj,
    ALU_done,
    R0_write_ALU, R0_read_ALU,
    R1_write_ALU, R1_read_ALU,
    R2_write_ALU, R2_read_ALU,
    R3_write_ALU, R3_read_ALU,
    P0_write_ALU, P0_read_ALU,
                    P1_read_ALU,
    ALU_opControl,
    ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read
);

ALUI_FSM ALUI_FSM_comp
(
    clk, reset, start_ALUI, opCode, Ri, Rj,
    bus,
    ALUI_done,
    R0_write_ALUI, R0_read_ALUI,
    R1_write_ALUI, R1_read_ALUI,
    R2_write_ALUI, R2_read_ALUI,
    R3_write_ALUI, R3_read_ALUI,

```

```

    P0_write_ALUI, P0_read_ALUI,
    ALUI_opControl,
    ALUI_alu_out_en, ALUI_writeIN1, ALUI_writeIN2, ALUI_read
);

Load Load_comp
(
    clk, reset, start_load, MFC, Ri, Rj,
    R0_read_load, R0_write_load,
    R1_read_load, R1_write_load,
    R2_read_load, R2_write_load,
    R3_read_load, R3_write_load,
    P0_read_load, P0_write_load,
    MAR_write_load, MAR_mem_read_load,
    MEM_RW_load, MEM_EN_load,
    MDR_mem_write_load, MDR_read_load,
    load_done
);

Store Store_comp
(
    clk, reset, start_store, MFC, Ri, Rj,
    R0_read_store,
    R1_read_store,
    R2_read_store,
    R3_read_store,
    P0_read_store,
    P1_read_Store,
    MAR_write_store, MAR_mem_read_store,
    MEM_RW_store, MEM_EN_store,
    MDR_mem_read_store, MDR_write_store,
    store_done
);

assign R0_read = R0_read_move || R0_read_ALU || R0_read_ALUI || R0_read_load ||
R0_read_store;
assign R1_read = R1_read_move || R1_read_ALU || R1_read_ALUI || R1_read_load ||
R1_read_store;
assign R2_read = R2_read_move || R2_read_ALU || R2_read_ALUI || R2_read_load ||
R2_read_store;
assign R3_read = R3_read_move || R3_read_ALU || R3_read_ALUI || R3_read_load ||
R3_read_store;
assign P0_read = P0_read_move || P0_read_ALU || P0_read_ALUI || P0_read_load ||
P0_read_store;
assign P1_read = P1_read_move || P1_read_ALU || P1_read_Store|| input_enable;

```

```

assign R0_write = R0_write_move || R0_write_movi || R0_write_ALU || R0_write_ALUI
|| R0_write_load;
assign R1_write = R1_write_move || R1_write_movi || R1_write_ALU || R1_write_ALUI
|| R1_write_load;
assign R2_write = R2_write_move || R2_write_movi || R2_write_ALU || R2_write_ALUI
|| R2_write_load;
assign R3_write = R3_write_move || R3_write_movi || R3_write_ALU || R3_write_ALUI
|| R3_write_load;
assign P0_write = P0_write_move || P0_write_movi || P0_write_ALU || P0_write_ALUI
|| P0_write_load;

assign read_ALU      = ALU_read      || ALUI_read;
assign writeIN1      = ALU_writeIN1  || ALUI_writeIN1;
assign writeIN2      = ALU_writeIN2  || ALUI_writeIN2;
assign alu_out_en    = ALU_alu_out_en || ALUI_alu_out_en;
assign opControl     = ALU_opControl | ALUI_opControl;

assign MAR_write     = MAR_write_fetch || MAR_write_load ||
MAR_write_store;
assign MAR_mem_read  = MAR_mem_read_fetch || MAR_mem_read_load ||
MAR_mem_read_store;
assign MEM_RW        = MEM_RW_fetch      || MEM_RW_load      || MEM_RW_store;
assign MEM_EN        = MEM_EN_fetch      || MEM_EN_load      || MEM_EN_store;
assign MDR_mem_write = MDR_mem_write_fetch || MDR_mem_write_load;
assign MDR_read      = MDR_read_fetch    || MDR_read_load;
// assign MDR_mem_read = MDR_mem_read_store;
// assign MDR_write    = MDR_write_store;

ALU ALU_comp (clk, reset, bus, bus, read_ALU, writeIN1, writeIN2, alu_out_en,
opControl);
R0 R0_comp (clk, reset, bus, bus, R0_read, R0_write);
R1 R1_comp (clk, reset, bus, bus, R1_read, R1_write);
R2 R2_comp (clk, reset, bus, bus, R2_read, R2_write);
R3 R3_comp (clk, reset, bus, bus, R3_read, R3_write);
Port0 P0_comp (clk, reset, bus, bus, P0_read, P0_write, output_pin);
Port1 P1_comp (clk, reset, bus, P1_read, input_pin);
PC PC_comp (clk, reset, bus, PC_read, PC_increment);
MAR MAR_comp (clk, reset, bus, MAR_to_MEM, MAR_write, MAR_mem_read);
MEM MEM_comp (MEM_to_MDR, MFC, MEM_EN, MAR_to_MEM, MDR_to_MEM, MEM_RW);
MDR MDR_comp (clk, reset, bus, bus, MDR_read, MDR_write_store, MEM_to_MDR ,
MDR_to_MEM, MDR_mem_read_store, MDR_mem_write);
IR IR_comp (clk, reset, bus, out_to_decoder, IR_write, 1);
endmodule

```

Top\_tb.v

```
`timescale 1ns/1ps

module top_tb;

//inputs
reg clk, reset, input_enable;
reg[15:0] input_pin;
wire[15:0] output_pin;

top topTB(clk, reset, input_pin, output_pin, input_enable);

initial // Clock generator
begin
    clk = 0;
    forever #10 clk = !clk;
end

initial
begin

input_enable = 0;
input_pin = 16'hf0f0;
reset = 0;
#5 reset = 1;
#5 reset = 0;

#1800

input_enable = 1;
end

endmodule
```

## Fetch.v

```
module Fetch
(
    clk, reset, start, MFC,
    PC_read, PC_increment,
    MAR_write, MAR_mem_read,
    MEM_RW, MEM_EN,
    MDR_mem_write, MDR_read,
    IR_write, done
);

input clk, reset, start, MFC;
output reg PC_read, PC_increment;
output reg MAR_write, MAR_mem_read;
output reg MEM_RW, MEM_EN;
output reg MDR_mem_write, MDR_read;
output reg IR_write;
output reg done;

reg[2:0] pres_state, next_state;
parameter init = 0, st0 = 1, st1 = 2, st2 = 3, st3 = 4, WAIT1 = 5, DONE = 6;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= init;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample

//FSM next state logic
always @(pres_state or MFC or start)
begin: fsm
    case (pres_state)

        init: if(start) next_state <= st0;

        st0: next_state <= st1;

        st1: next_state <= WAIT1;

        WAIT1: if(!MFC) next_state <= st2;

        st2: next_state <= st3;
```

```

    st3: next_state <= DONE;

    DONE: next_state <= init;

    default: next_state<= init;

endcase end //fsm
//Moore output definition using pres_state only
always @(pres_state)
begin: outputs
    case (pres_state)

        init: begin
            PC_read          <= 0;
            MAR_write        <= 0;
            MAR_mem_read     <= 0;
            MEM_RW           <= 0;
            MEM_EN           <= 0;
            MDR_mem_write    <= 0;
            MDR_read         <= 0;
            IR_write         <= 0;
            PC_increment     <= 0;
            done <= 0;
        end

        st0: begin
            PC_read          <= 1;
            MAR_write        <= 1;
            MAR_mem_read     <= 0;
            MEM_RW           <= 0;
            MEM_EN           <= 0;
            MDR_mem_write    <= 0;
            MDR_read         <= 0;
            IR_write         <= 0;
            PC_increment     <= 0;
        end

        st1: begin
            PC_read          <= 0;
            MAR_write        <= 0;
            MAR_mem_read     <= 1;
            MEM_RW           <= 1;
            MEM_EN           <= 1;
            MDR_mem_write    <= 0;
            MDR_read         <= 0;
        end
    endcase
end

```



```

        IR_write      <= 0;
        PC_increment   <= 0;
    end

WAIT1: begin
    // PC_read      <= 0;
    // MAR_write     <= 0;
    // MAR_mem_read  <= 0;
    // MEM_RW        <= 0;
    // MEM_EN        <= 0;
    // MDR_mem_write <= 0;
    // MDR_read      <= 0;
    // IR_write      <= 0;
    // PC_increment   <= 0;
end

st2: begin
    PC_read      <= 0;
    MAR_write    <= 0;
    MAR_mem_read <= 0;
    MEM_RW       <= 0;
    MEM_EN       <= 0;
    MDR_mem_write <= 1;
    MDR_read     <= 0;
    IR_write     <= 0;
    PC_increment <= 0;
end

st3: begin
    PC_read      <= 0;
    MAR_write    <= 0;
    MAR_mem_read <= 0;
    MEM_RW       <= 0;
    MEM_EN       <= 0;
    MDR_mem_write <= 0;
    MDR_read     <= 1;
    IR_write     <= 1;

end

DONE: begin
    PC_read      <= 0;
    MAR_write    <= 0;
    MAR_mem_read <= 0;
    MEM_RW       <= 0;

```

```

        MEM_EN          <= 0;
        MDR_mem_write   <= 0;
        MDR_read        <= 0;
        IR_write        <= 0;
        done <= 1;
        PC_increment    <= 1;
    end

endcase
end //fsm

endmodule

```

Fetch\_tb.v

```

`timescale 1ns/1ps

module Fetch_tb;

reg clk, reset, start, MFC;
wire PC_read;
wire MAR_write, MAR_mem_read;
wire MEM_RW, MEM_EN;
wire MDR_mem_write, MDR_read;
wire IR_write;

Fetch_TB
(
    clk, reset, start, MFC,
    PC_read,
    MAR_write, MAR_mem_read,
    MEM_RW, MEM_EN,
    MDR_mem_write, MDR_read,
    IR_write
);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial

```

```

begin

    reset = 0;
    MFC = 1;
    start = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #10 start = 0;

    #100 MFC = 0;
    #1 MFC = 1;

    #100 start = 1;
    #5 start = 0;

    #200 MFC = 0;

end

endmodule

```

Move.v

```

module Move
(
    clk, reset, start, Ri, Rj,
    done,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read,
    P0_write, P0_read,
    P1_read
);

input clk, reset, start;
input[5:0] Ri, Rj;

output reg R0_write, R0_read;

```

```

output reg R1_write, R1_read;
output reg R2_write, R2_read;
output reg R3_write, R3_read;
output reg P0_write, P0_read;
output reg P1_read;

output reg done;

reg[1:0] pres_state, next_state;
parameter INIT = 0, MAIN = 1, NEXT_I = 2;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= INIT;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample

//FSM next state logic
always @(pres_state or start)
begin: fsm
    case (pres_state)

        INIT: begin
            if(start) next_state <= MAIN;
            else next_state <= INIT;
        end
        MAIN: next_state <= NEXT_I;
        NEXT_I: next_state <= INIT;
        default: next_state<= INIT;

    endcase end //fsm

always @(pres_state)
begin: outputs
    case (pres_state)
        INIT: begin

            R0_write <= 0; R0_read <= 0;
            R1_write <= 0; R1_read <= 0;
            R2_write <= 0; R2_read <= 0;
            R3_write <= 0; R3_read <= 0;
            P0_write <= 0; P0_read <= 0;

```

```

        P1_read  <= 0;
        done <= 0;

    end

    MAIN: begin

        case(Ri)
            0: R0_write <= 1;
            1: R1_write <= 1;
            2: R2_write <= 1;
            3: R3_write <= 1;
            4: P0_write <= 1;
        endcase

        case(Rj)
            0: R0_read <= 1;
            1: R1_read <= 1;
            2: R2_read <= 1;
            3: R3_read <= 1;
            4: P0_read <= 1;
            5: P1_read <= 1;
        endcase
    end

    NEXT_I: begin
        R0_write <= 0; R0_read <= 0;
        R1_write <= 0; R1_read <= 0;
        R2_write <= 0; R2_read <= 0;
        R3_write <= 0; R3_read <= 0;
        P0_write <= 0; P0_read <= 0;
        P1_read  <= 0;
        done <= 1;
    end

endcase
end //fsm
endmodule

```

Move\_tb.v

```

`timescale 1ns/1ps

module Move_tb;

```

```

reg clk, reset, start;
reg[5:0] Ri, Rj;

wire R0_write, R0_read;
wire R1_write, R1_read;
wire R2_write, R2_read;
wire R3_write, R3_read;

Move TB
(
    clk, reset, start, Ri, Rj,
    start_next_I,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read
);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial
begin

    Ri = 0;
    Rj = 3;
    start = 0;
    reset = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #4 start = 0;

end

endmodule

```

Movi.v

```
// 0111 Ri Rj
module Movi
(
    clk, reset, start, Ri, num,
    out_to_bus,
    done,
    R0_write,
    R1_write,
    R2_write,
    R3_write,
    P0_write
);

input clk, reset, start;
input[5:0] Ri, num;

output reg R0_write;
output reg R1_write;
output reg R2_write;
output reg R3_write;
output reg P0_write;
output reg done;

output[15:0] out_to_bus;

reg[1:0] pres_state, next_state;

reg read;

parameter INIT = 0, MAIN = 1, NEXT_I = 2;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= INIT;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample

//FSM next state logic
always @(pres_state or start)
    begin: fsm
        case (pres_state)
```

```

INIT: begin
    if(start) next_state <= MAIN;
    else next_state <= INIT;
end
MAIN: next_state <= NEXT_I;
NEXT_I: next_state <= INIT;
default: next_state<= INIT;

endcase end //fsm

```

```

always @(pres_state)
begin: outputs
    case (pres_state)
    INIT: begin

        R0_write <= 0;
        R1_write <= 0;
        R2_write <= 0;
        R3_write <= 0;
        P0_write <= 0;
        read <= 0;
        done <= 0;

    end

    MAIN: begin

        case(Ri)
            0: R0_write <= 1;
            1: R1_write <= 1;
            2: R2_write <= 1;
            3: R3_write <= 1;
            4: P0_write <= 1;
        endcase

        read <= 1;

    end

    NEXT_I: begin
        R0_write <= 0;
        R1_write <= 0;
        R2_write <= 0;
        R3_write <= 0;

```



```

        R0_write <= 0;
        read <= 0;
        done <= 1;
    end

    endcase
end //fsm

assign out_to_bus = read? num : 16'hzzzz;

endmodule

```

Movi\_tb.v

```

`timescale 1ns/1ps

module Movi_tb;

reg clk, reset, start;
reg[5:0] Ri, num;

wire R0_write;
wire R1_write;
wire R2_write;
wire R3_write;
wire[15:0] out_to_bus;

Movi TB
(
    clk, reset, start, Ri, num,
    out_to_bus,
    start_next_I,
    R0_write,
    R1_write,
    R2_write,
    R3_write
);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

```

```

initial

begin

    Ri = 0;
    num = 15;
    start = 0;
    reset = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #4 start = 0;

end

endmodule

```

ALU\_FSM.v

```

// 0111 Ri Rj

module ALU_FSM
(
    clk, reset, start, opCode, Ri, Rj,
    done,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read,
    P0_write, P0_read,
    P1_read,
    ALU_opControl,
    ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read
);

input clk, reset, start;
input[3:0] opCode;
input[5:0] Ri, Rj;

output reg R0_write, R0_read;
output reg R1_write, R1_read;
output reg R2_write, R2_read;
output reg R3_write, R3_read;

```

```

output reg P0_write, P0_read;
output reg P1_read;

output reg[2:0] ALU_opControl;
output reg ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read;
output reg done;

reg[2:0] pres_state, next_state;
parameter INIT = 0, IN1 = 1, IN2 = 2, EVAL = 3, OUT = 4, NEXT_I = 5;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= INIT;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample

//FSM next state logic
always @(pres_state or start)
begin: fsm
    case (pres_state)

        INIT: begin
            if(start) next_state <= IN1;
            else next_state <= INIT;
        end
        IN1: next_state <= IN2;
        IN2: next_state <= EVAL;
        EVAL: next_state <= OUT;
        OUT: next_state <= NEXT_I;
        NEXT_I: next_state <= INIT;
        default: next_state<= INIT;

    endcase end //fsm

always @(pres_state)
begin: outputs
    case (pres_state)
        INIT: begin

            R0_write <= 0; R0_read <= 0;
            R1_write <= 0; R1_read <= 0;
            R2_write <= 0; R2_read <= 0;

```

```

R3_write <= 0; R3_read <= 0;
P0_write <= 0; P0_read <= 0;
P1_read <= 0;
ALU_opControl <= 0;
ALU_alu_out_en <= 0; ALU_writeIN1 <= 0; ALU_writeIN2 <= 0; ALU_read <=
0;

done <= 0;

end

IN1: begin

    //////////////////////////////////
    R0_write <= 0;
    R1_write <= 0;
    R2_write <= 0;
    R3_write <= 0;
    P0_write <= 0;
    P1_read <= 0;
    ALU_opControl <= 0;
    ALU_alu_out_en <= 0; ALU_writeIN2 <= 0; ALU_read <= 0;
    //////////////////////////////////
    case(Ri)
        0: R0_read <= 1;
        1: R1_read <= 1;
        2: R2_read <= 1;
        3: R3_read <= 1;
        4: P0_read <= 1;
    endcase

    ALU_writeIN1 <= 1;

end

IN2: begin

    //may be redundant
    R0_write <= 0;
    R1_write <= 0;
    R2_write <= 0;
    R3_write <= 0;
    P0_write <= 0;
    ALU_opControl <= 0;
    ALU_alu_out_en <= 0; ALU_writeIN1 <= 0; ALU_read <= 0;

```

```

        case(Ri)
            0: R0_read <= 0;
            1: R1_read <= 0;
            2: R2_read <= 0;
            3: R3_read <= 0;
            4: P0_read <= 0;
        endcase
        //////////////////////////////////

        case(Rj)
            0: R0_read <= 1;
            1: R1_read <= 1;
            2: R2_read <= 1;
            3: R3_read <= 1;
            4: P0_read <= 1;
            5: P1_read <= 1;
        endcase

        ALU_writeIN2 <= 1;

    end

    EVAL: begin //if ALU_IN1 or ALU_IN2 changed at this phase the output will
change as well because they are not set to zero in this state
        //////////////////////////////////
        R0_write <= 0; R0_read <= 0;
        R1_write <= 0; R1_read <= 0;
        R2_write <= 0; R2_read <= 0;
        R3_write <= 0; R3_read <= 0;
        P0_write <= 0; P0_read <= 0;
        P1_read <= 0;
        ALU_writeIN1 <= 0; ALU_writeIN2 <= 0; ALU_read <= 0;
        //////////////////////////////////
        ALU_alu_out_en <= 1;

        ALU_opControl <= opCode[2:0];

    end

    OUT: begin
        //////////////////////////////////
        R0_read <= 0;
        R1_read <= 0;
        R2_read <= 0;
        R3_read <= 0;

```

```

        P0_read <= 0;
        P1_read <= 0;
        ALU_opControl <= 0;
        ALU_alu_out_en <= 0; ALU_writeIN1 <=0; ALU_writeIN2 <= 0;
        //////////////////////////////////////

        ALU_read <= 1;

        case(Ri)
            0: R0_write <= 1;
            1: R1_write <= 1;
            2: R2_write <= 1;
            3: R3_write <= 1;
            4: P0_write <= 1;
        endcase
    end

    NEXT_I: begin
        R0_write <= 0; R0_read <= 0;
        R1_write <= 0; R1_read <= 0;
        R2_write <= 0; R2_read <= 0;
        R3_write <= 0; R3_read <= 0;
        P0_write <= 0; P0_read <= 0;
        P1_read <= 0;
        ALU_opControl <= 0;
        ALU_alu_out_en <= 0; ALU_writeIN1 <=0; ALU_writeIN2 <= 0; ALU_read <=
0;
        done <= 1;
    end

    endcase
end //fsm

endmodule

```

ALU\_FSM\_tb.v

```

`timescale 1ns/1ps

module ALU_FSM_tb;

    reg clk, reset, start;
    reg[3:0] opCode;
    reg[5:0] Ri, Rj;

```

```

wire R0_write, R0_read;
wire R1_write, R1_read;
wire R2_write, R2_read;
wire R3_write, R3_read;

wire[2:0] ALU_opControl;
wire ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read;
wire done;

ALU_FSM TB
(
    clk, reset, start, opCode, Ri, Rj,
    done,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read,
    ALU_opControl,
    ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read
);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial
begin
    Ri = 0;
    Rj = 3;
    opCode = 1;
    start = 0;
    reset = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #4 start = 0;

end

endmodule

```

ALUI\_FSM.v

```
// 0111 Ri Rj

module ALUI_FSM
(
    clk, reset, start, opCode, Ri, num,
    out_to_bus,
    done,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read,
    P0_write, P0_read,
    ALU_opControl,
    ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read
);

input clk, reset, start;
input[3:0] opCode;
input[5:0] Ri, num;

output reg R0_write, R0_read;
output reg R1_write, R1_read;
output reg R2_write, R2_read;
output reg R3_write, R3_read;
output reg P0_write, P0_read;
output reg[2:0] ALU_opControl;
output reg ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read;
output reg done;

output[15:0] out_to_bus;

reg read;

reg[2:0] pres_state, next_state;
parameter INIT = 0, IN1 = 1, IN2 = 2, EVAL = 3, OUT = 4, NEXT_I = 5;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= INIT;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample
```



```

//FSM next state logic
always @(pres_state or start)
begin: fsm
    case (pres_state)

        INIT: begin
            if(start) next_state <= IN1;
            else next_state <= INIT;
        end
        IN1:  next_state <= IN2;
        IN2:  next_state <= EVAL;
        EVAL: next_state <= OUT;
        OUT:  next_state <= NEXT_I;
        NEXT_I: next_state <= INIT;
        default: next_state <= INIT;

    endcase end //fsm

always @(pres_state)
begin: outputs
    case (pres_state)
        INIT: begin

            R0_write <= 0; R0_read <= 0;
            R1_write <= 0; R1_read <= 0;
            R2_write <= 0; R2_read <= 0;
            R3_write <= 0; R3_read <= 0;
            P0_write <= 0; P0_read <= 0;
            ALU_opControl <= 0;
            ALU_alu_out_en <= 0; ALU_writeIN1 <= 0; ALU_writeIN2 <= 0; ALU_read <=
0;

            read <= 0;
            done <= 0;

        end

        IN1: begin

            ///////////
            R0_write <= 0;
            R1_write <= 0;
            R2_write <= 0;
            R3_write <= 0;
            P0_write <= 0;

```

```

    ALU_opControl <= 0;
    ALU_alu_out_en <= 0; ALU_writeIN2 <= 0; ALU_read <= 0;
    read <= 0;
    //////////////////////////////////
    case(Ri)
        0: R0_read <= 1;
        1: R1_read <= 1;
        2: R2_read <= 1;
        3: R3_read <= 1;
        4: P0_read <= 1;
    endcase

    ALU_writeIN1 <= 1;

end

```

```

IN2: begin

    //may be redundant
    R0_write <= 0;
    R1_write <= 0;
    R2_write <= 0;
    R3_write <= 0;
    P0_write <= 0;
    ALU_opControl <= 0;
    ALU_alu_out_en <= 0; ALU_writeIN1 <= 0; ALU_read <= 0;

    case(Ri)
        0: R0_read <= 0;
        1: R1_read <= 0;
        2: R2_read <= 0;
        3: R3_read <= 0;
        4: P0_read <= 0;
    endcase
    //////////////////////////////////

    read <= 1;

    ALU_writeIN2 <= 1;

end

```

```

    EVAL: begin //if ALU_IN1 or ALU_IN2 changed at this phase the output will
change as well because they are not set to zero in this state
    //////////////////////////////////

```

```

R0_write <= 0; R0_read <= 0;
R1_write <= 0; R1_read <= 0;
R2_write <= 0; R2_read <= 0;
R3_write <= 0; R3_read <= 0;
P0_write <= 0; P0_read <= 0;
ALU_writeIN1 <=0; ALU_writeIN2 <= 0; ALU_read <= 0;
read <= 0;
////////////////////////////////////

ALU_alu_out_en <= 1;

ALU_opControl <= opCode;

end

OUT: begin
    //////////////////////////////////
    R0_read <= 0;
    R1_read <= 0;
    R2_read <= 0;
    R3_read <= 0;
    P0_read <= 0;
    ALU_opControl <= 0;
    ALU_alu_out_en <= 0; ALU_writeIN1 <=0; ALU_writeIN2 <= 0;
    read <= 0;
    //////////////////////////////////

    ALU_read <= 1;

    case(Ri)
        0: R0_write <= 1;
        1: R1_write <= 1;
        2: R2_write <= 1;
        3: R3_write <= 1;
        4: P0_write <= 1;
    endcase
end

NEXT_I: begin
    R0_write <= 0; R0_read <= 0;
    R1_write <= 0; R1_read <= 0;
    R2_write <= 0; R2_read <= 0;
    R3_write <= 0; R3_read <= 0;
    P0_write <= 0; P0_read <= 0;
    ALU_opControl <= 0;

```

```

        ALU_alu_out_en <= 0; ALU_writeIN1 <=0; ALU_writeIN2 <= 0; ALU_read <=
0;

        read <= 0;
        done <= 1;
    end

    endcase
end //fsm

assign out_to_bus = read? num : 16'hzzzz;

endmodule

```

ALUI\_FSM\_tb.v

```

`timescale 1ns/1ps

module ALUI_FSM_tb;

reg clk, reset, start;
reg[3:0] opCode;
reg[5:0] Ri, num;

wire R0_write, R0_read;
wire R1_write, R1_read;
wire R2_write, R2_read;
wire R3_write, R3_read;

wire[2:0] ALU_opControl;
wire ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read;
wire done;
wire[15:0] out_to_bus;

ALUI_FSM TB
(
    clk, reset, start, opCode, Ri, num,
    out_to_bus,
    done,
    R0_write, R0_read,
    R1_write, R1_read,
    R2_write, R2_read,
    R3_write, R3_read,
    ALU_opControl,
    ALU_alu_out_en, ALU_writeIN1, ALU_writeIN2, ALU_read
);

```

```

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial

begin

    Ri = 0;
    num = 6'b111111;
    opCode = 5;
    start = 0;
    reset = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #4 start = 0;

end

endmodule

```

Store.v

```

module Store
(
    clk, reset, start, MFC, Ri, Rj,
    R0_read,
    R1_read,
    R2_read,
    R3_read,
    P0_read,
    P1_read,
    MAR_write, MAR_mem_read,
    MEM_RW, MEM_EN,
    MDR_mem_read, MDR_write,
    done
);

```

```

input clk, reset, start, MFC;
input[5:0] Ri, Rj;

output reg R0_read;
output reg R1_read;
output reg R2_read;
output reg R3_read;
output reg P0_read;
output reg P1_read;
output reg MAR_write, MAR_mem_read;
output reg MEM_RW, MEM_EN;
output reg MDR_mem_read, MDR_write;
output reg done;

reg[2:0] pres_state, next_state;
parameter st0 = 0, st1 = 1, st2 = 2, WAIT1 = 4, init = 5, DONE = 6;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= init;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample

//FSM next state logic
always @(pres_state or MFC or start)
begin: fsm
    case (pres_state)

        init: begin
            if(start) next_state <= st0;
            else next_state <= init;
        end

        st0: next_state <= st1;

        st1: next_state <= st2;

        st2: next_state <= WAIT1;

        WAIT1: if(!MFC) next_state <= DONE;

        DONE: next_state <= init;
    endcase
end

```

```

        default: next_state<= init;

    endcase end //fsm

//Moore output definition using pres_state only
always @(pres_state)
begin: outputs
    case (pres_state)

        init: begin

            R0_read    <= 0;
            R1_read    <= 0;
            R2_read    <= 0;
            R3_read    <= 0;
            P0_read    <= 0;
            P1_read    <= 0;
            MAR_write  <= 0; MAR_mem_read <= 0;
            MEM_RW     <= 0; MEM_EN      <= 0;
            MDR_mem_read <= 0; MDR_write  <= 0;
            done <= 0;

        end

        st0: begin

            case(Ri)

                0: R0_read <= 1;
                1: R1_read <= 1;
                2: R2_read <= 1;
                3: R3_read <= 1;
                4: P0_read <= 1;
                5: P1_read <= 1;

            endcase

            MAR_write  <= 0; MAR_mem_read <= 0;
            MEM_RW     <= 0; MEM_EN      <= 0;
            MDR_mem_read <= 0; MDR_write  <= 1;

        end

        st1: begin

```

```

    case(Ri)

    0: R0_read <= 0;
    1: R1_read <= 0;
    2: R2_read <= 0;
    3: R3_read <= 0;
    4: P0_read <= 0;
    5: P1_read <= 0;

endcase

case(Rj)

    0: R0_read <= 1;
    1: R1_read <= 1;
    2: R2_read <= 1;
    3: R3_read <= 1;
    4: P0_read <= 1;
    5: P1_read <= 1;

endcase

MAR_write    <= 1; MAR_mem_read <= 0;
MEM_RW       <= 0; MEM_EN      <= 0;
MDR_mem_read <= 0; MDR_write   <= 0;

end

st2: begin
    R0_read    <= 0;
    R1_read    <= 0;
    R2_read    <= 0;
    R3_read    <= 0;
    P0_read    <= 0;
    P1_read    <= 0;
    MAR_write  <= 0; MAR_mem_read <= 1;
    MEM_RW     <= 0; MEM_EN      <= 1;
    MDR_mem_read <= 1; MDR_write  <= 0;
end

WAIT1: begin

    // R0_read    <= 0;
    // R1_read    <= 0;
    // R2_read    <= 0;

```



```

        // R3_read      <= 0;
        // P0_read      <= 0;
        // P1_read      <= 0;
        // MAR_write    <= 0; MAR_mem_read <= 0;
        // MEM_RW       <= 0; MEM_EN      <= 0;
        // MDR_mem_read <= 0; MDR_write   <= 0;

    end

    DONE: begin

        R0_read      <= 0;
        R1_read      <= 0;
        R2_read      <= 0;
        R3_read      <= 0;
        P0_read      <= 0;
        P1_read      <= 0;
        MAR_write    <= 0; MAR_mem_read <= 0;
        MEM_RW       <= 0; MEM_EN      <= 0;
        MDR_mem_read <= 0; MDR_write   <= 0;
        done <= 0;
        done <= 1;

    end

endcase
end //fsm

endmodule

```

Store\_tb.v

```

`timescale 1ns/1ps

module Store_tb;

    reg clk, reset, start, MFC;
    reg[5:0] Ri, Rj;
    wire R0_read;
    wire R1_read;
    wire R2_read;
    wire R3_read;
    wire P0_read;
    wire MAR_write, MAR_mem_read;
    wire MEM_RW, MEM_EN;

```

```

wire MDR_mem_read, MDR_write;
wire done;

Store TB
(
    clk, reset, start, MFC, Ri, Rj,
    R0_read,
    R1_read,
    R2_read,
    R3_read,
    P0_read,
    MAR_write, MAR_mem_read,
    MEM_RW, MEM_EN,
    MDR_mem_read, MDR_write,
    done
);

```

```

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

```

```

initial

```

```

begin

    reset = 0;
    MFC = 1;
    start = 0;
    Ri = 6'hfffffff;
    Rj = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #10 start = 0;

    #100 MFC = 0;
    #1 MFC = 1;

    #100 start = 1;
    #5 start = 0;

    #200 MFC = 0;

```

```
end
```

```
endmodule
```

Load.v

```
module Load
(
    clk, reset, start, MFC, Ri, Rj,
    R0_read, R0_write,
    R1_read, R1_write,
    R2_read, R2_write,
    R3_read, R3_write,
    P0_read, P0_write,
    MAR_write, MAR_mem_read,
    MEM_RW, MEM_EN,
    MDR_mem_write, MDR_read,
    done
);

input clk, reset, start, MFC;
input[5:0] Ri, Rj;

output reg R0_read, R0_write;
output reg R1_read, R1_write;
output reg R2_read, R2_write;
output reg R3_read, R3_write;
output reg P0_read, P0_write;
output reg MAR_write, MAR_mem_read;
output reg MEM_RW, MEM_EN;
output reg MDR_mem_write, MDR_read;
output reg done;

reg[2:0] pres_state, next_state;
parameter st0 = 0, st1 = 1, st2 = 2, st3 = 3, WAIT1 = 4, init = 5, DONE = 6;

//FSM register
always @(posedge clk or posedge reset)
    begin:statereg
        if (reset) pres_state <= init;
        else pres_state <= next_state;
    end //stateregFSM Description by VerilogExample
```

```

//FSM next state logic
always @(pres_state or MFC or start)
begin: fsm
    case (pres_state)

        init: begin
            if(start) next_state <= st0;
            else next_state <= init;
        end

        st0: next_state <= st1;

        st1: next_state <= WAIT1;

        WAIT1: if(!MFC) next_state <= st2;

        st2: next_state <= st3;

        st3: next_state <= DONE;

        DONE: next_state <= init;

        default: next_state<= init;

    endcase end //fsm

//Moore output definition using pres_state only
always @(pres_state)
begin: outputs
    case (pres_state)

        init: begin
            R0_write <= 0; R0_read <= 0;
            R1_write <= 0; R1_read <= 0;
            R2_write <= 0; R2_read <= 0;
            R3_write <= 0; R3_read <= 0;
            P0_write <= 0; P0_read <= 0;
            MAR_write <= 0; MAR_mem_read <= 0;
            MEM_RW <= 0; MEM_EN <= 0;
            MDR_mem_write <= 0;

            MDR_read <= 0;
            done <= 0;
        end
    endcase
end

```

```

st0: begin

    R0_write <= 0;
    R1_write <= 0;
    R2_write <= 0;
    R3_write <= 0;
    P0_write <= 0;

    case(Ri)

        0: R0_read <= 1;
        1: R1_read <= 1;
        2: R2_read <= 1;
        3: R3_read <= 1;
        4: P0_read <= 1;

    endcase

    MAR_write      <= 1; MAR_mem_read  <= 0;
    MEM_RW         <= 0; MEM_EN       <= 0;
                                     MDR_mem_write <= 0;
    MDR_read       <= 0;

    end

st1: begin

    R0_write <= 0; R0_read <= 0;
    R1_write <= 0; R1_read <= 0;
    R2_write <= 0; R2_read <= 0;
    R3_write <= 0; R3_read <= 0;
    P0_write <= 0; P0_read <= 0;
    MAR_write      <= 0; MAR_mem_read  <= 1;
    MEM_RW         <= 1; MEM_EN       <= 1;
                                     MDR_mem_write <= 0;
    MDR_read       <= 0;

    end

WAIT1: begin

    // R0_write <= 0; R0_read <= 0;
    // R1_write <= 0; R1_read <= 0;
    // R2_write <= 0; R2_read <= 0;
    // R3_write <= 0; R3_read <= 0;

```

```

        // P0_write <= 0; P0_read <= 0;
        // MAR_write      <= 0; MAR_mem_read  <= 0;
        // MEM_RW          <= 0; MEM_EN       <= 0;
        //                  MDR_mem_write <= 0;
        // MDR_read        <= 0;

end

st2: begin
    R0_write <= 0; R0_read <= 0;
    R1_write <= 0; R1_read <= 0;
    R2_write <= 0; R2_read <= 0;
    R3_write <= 0; R3_read <= 0;
    P0_write <= 0; P0_read <= 0;
    MAR_write      <= 0; MAR_mem_read  <= 0;
    MEM_RW          <= 0; MEM_EN       <= 0;
                    MDR_mem_write <= 1;
    MDR_read        <= 0;
end

st3: begin

    R0_read <= 0;
    R1_read <= 0;
    R2_read <= 0;
    R3_read <= 0;
    P0_read <= 0;
    MAR_write      <= 0; MAR_mem_read  <= 0;
    MEM_RW          <= 0; MEM_EN       <= 0;
                    MDR_mem_write <= 0;
    MDR_read        <= 1;
    case(Rj)

        0: R0_write <= 1;
        1: R1_write <= 1;
        2: R2_write <= 1;
        3: R3_write <= 1;
        4: P0_write <= 1;

    endcase

end

DONE: begin

```

```

        R0_write <= 0; R0_read <= 0;
        R1_write <= 0; R1_read <= 0;
        R2_write <= 0; R2_read <= 0;
        R3_write <= 0; R3_read <= 0;
        P0_write <= 0; P0_read <= 0;
        MAR_write      <= 0; MAR_mem_read  <= 0;
        MEM_RW         <= 0; MEM_EN        <= 0;
                                MDR_mem_write <= 0;
        MDR_read       <= 0;

        done <= 1;
    end

endcase
end //fsm
endmodule

```

Load\_tb.v

```

`timescale 1ns/1ps

module Load_tb;

reg clk, reset, start, MFC;
reg[5:0] Ri, Rj;
wire R0_read, R0_write;
wire R1_read, R1_write;
wire R2_read, R2_write;
wire R3_read, R3_write;
wire P0_read, P0_write;
wire MAR_write, MAR_mem_read;
wire MEM_RW, MEM_EN;
wire MDR_mem_write, MDR_read;
wire done;

Load_TB
(
    clk, reset, start, MFC, Ri, Rj,
    R0_read, R0_write,
    R1_read, R1_write,
    R2_read, R2_write,
    R3_read, R3_write,
    P0_read, P0_write,
    MAR_write, MAR_mem_read,

```

```

        MEM_RW, MEM_EN,
        MDR_mem_write, MDR_read,
        done
    );

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial

begin

    reset = 0;
    MFC = 1;
    start = 0;
    Ri = 6'hfffffff;
    Rj = 0;
    #1 reset = 1;
    #1 reset = 0;
    #20 start = 1;
    #10 start = 0;

    #100 MFC = 0;
    #1 MFC = 1;

    #100 start = 1;
    #5 start = 0;

    #200 MFC = 0;

end

endmodule

```

ALU.v

```

//module ALU (reset, clk, in_from_bus, writeIN1, writeIN2, alu_out_en, read,
OpControl, out_to_bus);
module ALU (clk, reset, in_from_bus, out_to_bus, read, writeIN1, writeIN2,
alu_out_en, OpControl);

```



```

//parameters
parameter ADD = 0;
parameter SUB = 1;
parameter NOT = 2;
parameter AND = 3;
parameter OR = 4;
parameter XOR = 5;
parameter XNOR = 6;

//inputs
input clk;
input reset;
input[15:0] in_from_bus;
input writeIN1;
input writeIN2;
input alu_out_en;
input read;
input[2:0] OpControl;

//outputs
output [15:0] out_to_bus;

//internal signals
reg[15:0] IN1_reg;
reg[15:0] IN2_reg;
reg[15:0] OUT_reg;

always @(posedge clk or posedge reset)
begin
    if(reset) begin
        IN1_reg <= 0;
        IN2_reg <= 0;
    end
    else begin
        if(writeIN1) IN1_reg <= in_from_bus;
        if(writeIN2) IN2_reg <= in_from_bus;
    end
end

//implementation
always @(*)
begin
    if(reset) OUT_reg <= 0;
    else if(alu_out_en) begin
        case(OpControl)

```

```

        ADD:      OUT_reg <= IN1_reg + IN2_reg ;
        SUB:      OUT_reg <= IN1_reg - IN2_reg ;
        NOT:      OUT_reg <= ~IN1_reg          ;
        AND:      OUT_reg <= IN1_reg & IN2_reg ;
        OR:       OUT_reg <= IN1_reg | IN2_reg ;
        XOR:      OUT_reg <= IN1_reg ^ IN2_reg ;
        XNOR:     OUT_reg <= IN1_reg ~^ IN2_reg;
        default:  OUT_reg <= 16'h0000          ;
    endcase
end
end

assign out_to_bus = read? OUT_reg : 16'hzzzz;

endmodule

```

ALU\_tb.v

```

`timescale 1ns/1ps

module ALU_tb;

//parameters
parameter ADD  = 0;
parameter SUB  = 1;
parameter NOT  = 2;
parameter AND  = 3;
parameter OR   = 4;
parameter XOR  = 5;
parameter XNOR = 6;

//inputs
reg reset;
reg clk;
reg[15:0] Bus_in;
reg IN1_en;
reg IN2_en;
reg OUT_en;
reg OUT_reg_en;
reg[2:0] OpControl;

//outputs
wire[15:0] Bus_out;

```

```
ALU ALU_c (reset, clk, Bus_in, IN1_en, IN2_en, OUT_en, OUT_reg_en, OpControl, Bus_out);
```

```
initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end
```

```
initial
```

```
begin
```

```
    Bus_in = 16'h55;
    reset = 0;
    IN1_en = 0;
    IN2_en = 0;
    OUT_en = 0;
    OUT_reg_en = 0;
    OpControl = 0;
    #1
    reset = 1;
    #1
    reset = 0;
    IN1_en = 1;
    IN2_en = 1;
    OUT_en = 1;
    #10 OpControl = ADD;
    OUT_reg_en = 1;
    #10 OpControl = SUB;
    #10 OpControl = NOT;
    #10 OpControl = AND;
    #10 OpControl = OR;
    #10 OpControl = XOR;
    #10 OpControl = XNOR;
    #10 OpControl = 7;
    #10 OUT_en = 0;
    #10;
    $stop;
```

```
end
```

```
endmodule
```

## Decoder.v

```
module Decoder(enable, opCode, start_move, start_movi, start_ALU, start_ALUI,
start_load, start_store);

input enable;
input[3:0] opCode;

output reg start_move, start_movi, start_ALU, start_ALUI, start_load,
start_store;

always @(*)
begin
    if(enable) begin
        case(opCode)

            4'b0000: begin
                start_move <= 0;
                start_movi <= 0;
                start_ALU <= 1;
                start_ALUI <= 0;
                start_load <= 0;
                start_store<= 0;
            end
            4'b0001: begin
                start_move <= 0;
                start_movi <= 0;
                start_ALU <= 1;
                start_ALUI <= 0;
                start_load <= 0;
                start_store<= 0;
            end
            4'b0010: begin
                start_move <= 0;
                start_movi <= 0;
                start_ALU <= 1;
                start_ALUI <= 0;
                start_load <= 0;
                start_store<= 0;
            end
            4'b0011: begin
                start_move <= 0;
                start_movi <= 0;
                start_ALU <= 1;
                start_ALUI <= 0;
            end
        endcase
    end
end
```

```

        start_load <= 0;
        start_store<= 0;
    end
    4'b0100: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU   <= 1;
        start_ALUI  <= 0;
        start_load  <= 0;
        start_store<= 0;
    end
    4'b0101: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU   <= 1;
        start_ALUI  <= 0;
        start_load  <= 0;
        start_store<= 0;
    end
    4'b0110: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU   <= 1;
        start_ALUI  <= 0;
        start_load  <= 0;
        start_store<= 0;
    end

    4'b1000: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU   <= 0;
        start_ALUI  <= 1;
        start_load  <= 0;
        start_store<= 0;
    end

    4'b1001: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU   <= 0;
        start_ALUI  <= 1;
        start_load  <= 0;
        start_store<= 0;
    end
end

```

```

    4'b0111: begin
        start_move <= 1;
        start_movi <= 0;
        start_ALU  <= 0;
        start_ALUI <= 0;
        start_load <= 0;
        start_store<= 0;
    end
    4'b1111: begin
        start_move <= 0;
        start_movi <= 1;
        start_ALU  <= 0;
        start_ALUI <= 0;
        start_load <= 0;
        start_store<= 0;
    end

    4'b1010: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU  <= 0;
        start_ALUI <= 0;
        start_load <= 1;
        start_store<= 0;
    end

    4'b1011: begin
        start_move <= 0;
        start_movi <= 0;
        start_ALU  <= 0;
        start_ALUI <= 0;
        start_load <= 0;
        start_store<= 1;
    end

endcase
end
else begin
    start_move <= 0;
    start_movi <= 0;
    start_ALU  <= 0;
    start_ALUI <= 0;
    start_load <= 0;
    start_store<= 0;

```

```
    end
end

endmodule
```

IR.v

```
//module IR(clk, reset, write, FSM_read, in_from_bus, out_to_decoder); //FSM_read
is not necessary
module IR    (clk, reset, in_from_bus, out_to_decoder,        write, FSM_read);

input clk, reset, write, FSM_read;
input [15:0] in_from_bus;
output[15:0] out_to_decoder;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
end

//I may not need the FSM_read
assign out_to_decoder = FSM_read? register : 16'hzzzz;

endmodule
```

MAR.v

```
//module MAR(clk, reset, write, read, in_from_bus, out_to_mem); //read is not
necessary
module MAR    (clk, reset, in_from_bus, out_to_mem, write, mem_read);

input clk, reset, write, mem_read;
input [15:0] in_from_bus;
output[15:0] out_to_mem;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
```

```
end

assign out_to_mem = mem_read? register : 16'hzzzz;

endmodule
```

MAR\_tb.v

```
`timescale 1ns/1ns
module MAR_tb();

reg clk;
reg reset;
reg in_en;
reg out_en;
reg[15:0] data_in;
wire[15:0] data_out;

MAR TB(clk, reset, in_en, out_en, data_in, data_out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial
begin
    reset = 0;
    in_en = 0;
    out_en = 0;
    data_in = 16'hFFFF;
    out_en = 0;
    #5 reset = 1;
    #5 reset = 0;
    #10 out_en = 1;
        in_en = 1;
    #10 out_en = 0;

end
endmodule
```



MDR.v

```
//module MDR(clk, reset, write, mem_write, read, mem_read, in_from_bus,
out_to_bus, in_from_mem, out_to_mem);
module MDR (clk, reset, in_from_bus, out_to_bus, read, write, in_from_mem,
out_to_mem, mem_read, mem_write);

input clk, reset, write, mem_write, read, mem_read;
input[15:0] in_from_bus;
input[15:0] in_from_mem;

output[15:0] out_to_bus;
output[15:0] out_to_mem;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else begin//should make sure that one of them is enabled at a time
        if(write && !mem_write) register <= in_from_bus;
        if(mem_write && !write) register <= in_from_mem;
    end
end

assign out_to_bus = read? register: 16'hzzzz;
assign out_to_mem = mem_read? register : 16'hzzzz;

endmodule
```

MDR\_tb.v

```
`timescale 1ns/1ns
module MDR_tb();

//inputs
reg clk;
reg reset;
reg in_bus_en, in_mem_en, out_bus_en, out_mem_en;
reg[15:0] bus_in;
reg[15:0] mem_in;

//outputs
wire[15:0] bus_out;
```

```

wire[15:0] mem_out;

MDR TB(clk, reset, in_bus_en, in_mem_en, out_bus_en, out_mem_en, bus_in, bus_out,
mem_in, mem_out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial begin

reset = 0;
in_bus_en = 0; in_mem_en = 0; out_bus_en = 0; out_mem_en = 0;
bus_in = 1;
mem_in = 15;
#1 reset = 1;
#1 reset = 0;
in_bus_en = 1;
#20
in_bus_en = 0;
in_mem_en = 1;
out_bus_en = 1;
out_mem_en = 1;
#20
in_bus_en = 0; in_mem_en = 0; out_bus_en = 0; out_mem_en = 0;
reset = 1;
#1 reset = 0;

end
endmodule

```

PC.v

```

//module PC(clk, reset, increment, read, out_to_bus);
module PC (clk, reset, out_to_bus, read, increment);

input clk, reset, increment, read;

```

```

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(increment) register <= register + 1;
end

assign out_to_bus = read? register : 16'hzzzz;

endmodule

```

PC\_tb.v

```

`timescale 1ns/1ns
module PC_tb();

reg clk, reset, inc, out_en;

wire[15:0] data_out;

PC_TB(clk, reset, inc, out_en, data_out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial begin

reset = 0;
inc = 0;
out_en = 0;
#10
reset = 1;
#10
reset = 0;
out_en = 1;
#10

```

```

inc = 1;
#20 inc =0;

end
endmodule

```

Port0.v

```

//module Port0(clk, reset, read, write, in_from_bus, out_to_bus, out); //read is
for the tri state buffer
module Port0(clk, reset, in_from_bus, out_to_bus, read, write, out_pin);

input clk, reset, read, write; //read means read from the bus, the out_pin is
always out
input [15:0] in_from_bus;

output[15:0] out_to_bus;
output[15:0] out_pin;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus; //write into output when write == 1
end

assign out_pin = register;
assign out_to_bus = read? register : 16'hzzzz; //read from output when read == 1

endmodule

```

Port0\_tb.v

```

`timescale 1ns/1ns
module Port0_tb();

reg clk, reset, read, write;
reg[15:0] bus_in;

wire[15:0] bus_out;

```

```

wire[15:0] out;

Port0 TB(clk, reset, read, write, bus_in, bus_out, out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial begin

//as an output
read = 0;
write = 0;
reset = 0;
bus_in = 16'hffff;
#3 reset = 1;
#3 reset = 0;
#10 read = 1;
write = 1;
#10 read = 0;

end
endmodule

```

Port1.v

```

//module Port1(clk, reset, read, in, out_to_bus);
module Port1(clk, reset, out_to_bus, read, in_pin);

input clk, reset, read;
input[15:0] in_pin;

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;

```

```
    else register <= in_pin;
end

assign out_to_bus = read? register : 16'hzzzz;

endmodule
```

Port1\_tb.v

```
`timescale 1ns/1ns
module Port1_tb();
//bus_out means out to bus
reg clk, reset, read;
reg[15:0] in;

wire[15:0] bus_out;

Port1 TB(clk, reset, read, in, bus_out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial begin

//as an output
read = 0;
reset = 0;
in = 0;
#3 reset = 1;
#3 reset = 0;
in = 9;
#10 read = 1;
#10 read = 0;

end
endmodule
```

R0.v

```
//module R0(clk, reset, read, write, in_from_bus, out_to_bus);
module R0    (clk, reset, in_from_bus, out_to_bus, read, write);

input clk, reset, read, write;
input[15:0] in_from_bus;

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
end

assign out_to_bus = read? register : 16'hzzzz;

endmodule
```

R1.v

```
//module R0(clk, reset, read, write, in_from_bus, out_to_bus);
module R1    (clk, reset, in_from_bus, out_to_bus, read, write);

input clk, reset, read, write;
input[15:0] in_from_bus;

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
end

assign out_to_bus = read? register : 16'hzzzz;

endmodule
```

R2.v

```
//module R0(clk, reset, read, write, in_from_bus, out_to_bus);
module R2    (clk, reset, in_from_bus, out_to_bus, read, write);

input clk, reset, read, write;
input[15:0] in_from_bus;

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
end

assign out_to_bus = read? register : 16'hzzzz;

endmodule
```

R3.v

```
//module R0(clk, reset, read, write, in_from_bus, out_to_bus);
module R3    (clk, reset, in_from_bus, out_to_bus, read, write);

input clk, reset, read, write;
input[15:0] in_from_bus;

output[15:0] out_to_bus;

reg[15:0] register;

always@(posedge clk or posedge reset)
begin
    if(reset) register <= 0;
    else if(write) register <= in_from_bus;
end

assign out_to_bus = read? register : 16'hzzzz;
```



```
endmodule
```

R\_tb.v

```
`timescale 1ns/1ns
module R_tb();

reg clk, reset, read, write;
reg[15:0] bus_in;

wire[15:0] bus_out;
wire[15:0] out;

R0 TB(clk, reset, read, write, bus_in, bus_out);

initial // Clock generator
begin
    clk = 1;
    forever #10 clk = !clk;
end

initial begin

reset = 0;
read = 0;
write = 0;
bus_in = 0;
#10 reset = 1;
#3 reset = 0;
read = 1;
#15
bus_in = 15;
write = 1;

end
endmodule
```